

EG2300 — Engineering Design II

Program Counter with T Flip-Flops

Adding Unconditional Jump

1 Context

In Tutorial 14 you built a Program Counter using T flip-flops that can count up and reset to zero. In this workshop you will add **unconditional jump** functionality — the ability to load an arbitrary 4-bit address into the PC using the asynchronous set/clear pins. You will also need to ensure that your existing reset still works correctly *alongside* the new jump logic.

2 Learning Objectives

By the end of this workshop you should be able to:

1. Use the **asynchronous set/clear** pins on T flip-flops to load an arbitrary value (jump).
2. Modify existing reset logic so that reset and jump **coexist safely** (no Set/Clear conflicts).
3. Verify that **priority** is correct: reset overrides jump, jump overrides counting.

3 T Flip-Flop Recap

A T (toggle) flip-flop has the following behaviour:

T	Clock edge	Q (next)
0	↑	Q (hold)
1	↑	$\overline{Q}$ (toggle)

In Logisim the T flip-flop also has two **asynchronous** pins on the bottom:

Pin label	Name	Effect (active = 1)
1	Preset (Set)	Forces $Q = 1$ immediately, ignores clock
0	Clear (Reset)	Forces $Q = 0$ immediately, ignores clock

Important

If both the Set and Clear pins are driven high at the same time, Clear wins and Q is forced to **0**. While not an error in Logisim, this is **ambiguous behaviour** on real hardware — your logic should guarantee it never happens.

Experiment: See it for yourself. Before building the full counter, place a *single* T flip-flop and explore its three bottom pins.



Figure 1: $T = 1$ causes Q to toggle on every rising clock edge ($Q = 0 \rightarrow Q = 1$).

 


Figure 2: Async Set (pin “1”) forces $Q = 1$ without a clock edge.

 


Figure 3: Async Clear (pin “0”) forces $Q = 0$. Normal counting resumes when released.

 


Figure 4: Both Set and Clear active — Clear wins in Logisim ($Q = 0$), but undefined on real hardware.

4 Required Behaviour

The Program Counter is a 4-bit value stored across four T flip-flops. Three operations are possible, with the following **strict priority**:

Priority	Condition	Action	Mechanism
1 (highest)	$RST = 1$	$PC \leftarrow 0000$	Async clear all FFs
2	$JMP_EN = 1$	$PC \leftarrow ADDR$	Async set/clear per bit
3 (default)	Neither	$PC \leftarrow PC + 1$	T-input toggle chain

5 Interface Specification

Create a subcircuit called `ProgramCounter_TFF` with the following pins.

Name	Width	Dir.	Meaning
CLK	1	in	System clock (rising-edge)
RST	1	in	Asynchronous reset ($PC \leftarrow 0$)
JMP_EN	1	in	Jump enable
ADDR[3:0]	4	in	Jump target address
PC_OUT[3:0]	4	out	Current program counter value

6 Tasks

6.1 Part A — Starting Point

Goal: Verify your existing Program Counter from Tutorial 14 before modifying it.
You should already have:

- Four T flip-flops wired as a ripple-carry counter (counting 0–15).
- A RST input that clears all flip-flops to 0 (via the async Clear pins).

Test A.

- Toggle CLK manually — confirm output counts $0000 \rightarrow 0001 \rightarrow \dots \rightarrow 1111 \rightarrow 0000$.
- Assert RST — confirm output resets to 0000.
- If either is broken, fix it before proceeding.

6.2 Part B — Add Unconditional Jump

Goal: When JMP_EN is asserted, force the PC to the value on ADDR[3:0] using the async set/clear pins.

Currently your Clear pins are driven by RST alone. You will now use *both* the Set and Clear pins on each flip-flop to write an arbitrary address — while keeping reset working.

The problem. Your existing reset wires $\overline{\text{RST}}$ directly to every Clear pin. If you also wire jump logic to the Clear pins, you need to make sure:

1. Jump can drive both Set *and* Clear (to write 1s and 0s).
2. Reset still overrides jump (if both are active, reset wins).
3. Set and Clear are **never both high** on the same flip-flop.

Per-bit equations. For each bit $i \in \{0, 1, 2, 3\}$:

$$\text{SET}_i = \overline{\text{RST}} \text{ AND } \text{JMP_EN} \text{ AND } \text{ADDR}[i] \quad (1)$$

$$\text{CLR}_i = \text{RST} \text{ OR } (\text{JMP_EN} \text{ AND } \overline{\text{ADDR}[i]}) \quad (2)$$

- If $\text{ADDR}[i] = 1$ and $\text{RST} = 0$: Set fires $\Rightarrow Q_i = 1$.
- If $\text{ADDR}[i] = 0$: Clear fires $\Rightarrow Q_i = 0$.
- If $\text{RST} = 1$: Set is forced to 0, Clear is forced to 1 $\Rightarrow Q_i = 0$ regardless of jump. **Reset wins.**
- If $\text{JMP_EN} = 0$ and $\text{RST} = 0$: both pins are 0 $\Rightarrow$ normal clocked counting.

Design Note

Verify for yourself that SET_i and CLR_i can never both be 1:

- $\text{RST} = 1 \Rightarrow \text{SET}_i = 0$ (because of $\overline{\text{RST}}$), $\text{CLR}_i = 1$. ✓
- $\text{JMP_EN} = 1, \text{RST} = 0, \text{ADDR}[i] = 1 \Rightarrow \text{SET}_i = 1, \text{CLR}_i = 0$. ✓
- $\text{JMP_EN} = 1, \text{RST} = 0, \text{ADDR}[i] = 0 \Rightarrow \text{SET}_i = 0, \text{CLR}_i = 1$. ✓
- $\text{JMP_EN} = 0, \text{RST} = 0 \Rightarrow \text{SET}_i = 0, \text{CLR}_i = 0$. ✓

No conflict in any case.

Disable counting during jump. When JMP_EN is active, the T-inputs must be forced to 0 so the clock edge does not also toggle the flip-flops. Replace the constant 1 feeding T_0 :

$$T_0 = \overline{\text{JMP_EN}}$$

The carry chain naturally propagates the zero, since $T_1 = \overline{\text{JMP_EN}} \text{ AND } Q_0$, etc.

Design Note

Why disable T during a jump? The async pins override Q *instantly*, but the next clock edge would also toggle Q if $T = 1$. Without the NOT gate on T_0 , a jump to address A could immediately become $A + 1$ on the same clock edge — defeating the purpose of the jump.

Build instructions.

1. Add a 4-bit ADDR input pin and a splitter to break it into individual bits.
2. Add a JMP_EN input pin.
3. Add shared NOT gates: $\overline{\text{RST}}$ and $\overline{\text{JMP_EN}}$.
4. For each bit i , place:

- One NOT gate (inverts $\text{ADDR}[i]$).
 - One 3-input AND gate for SET_i (Equation 1: $\overline{\text{RST}}$, JMP_EN , $\text{ADDR}[i]$).
 - One 2-input AND gate for the inner term (JMP_EN AND $\overline{\text{ADDR}[i]}$).
 - One 2-input OR gate for CLR_i (Equation 2: RST OR inner).
5. Wire SET_i to the flip-flop's "1" pin.
 6. **Replace** the existing direct $\text{RST} \rightarrow \text{Clear}$ wire with CLR_i from the OR gate.
 7. Replace the constant 1 on T_0 with $\overline{\text{JMP_EN}}$.

Test B.

- Let the counter run to some value (e.g. 0011).
- Set $\text{ADDR} = 1010$ and pulse JMP_EN .
- Verify PC_OUT immediately shows 1010.
- Release JMP_EN and clock again — counter resumes from 1011.

 


Figure 5: Jump active — $\text{ADDR} = 1010$, $\text{JMP_EN} = 1$. PC_OUT shows 1010; T-inputs are forced to 0.

 


Figure 6: After releasing JMP_EN and clocking once, the counter resumes from the loaded value.

6.3 Part C — Verify Priority

Goal: Confirm that reset, jump, and counting interact correctly.

Test C — reset overrides jump.

- Run counter to 0110.
- Assert RST. Verify PC_OUT = 0000 immediately.
- While RST is held, also assert JMP_EN with ADDR = 1111. Verify PC_OUT **stays 0000** (reset wins).
- Release RST (keep JMP_EN high). Verify PC_OUT jumps to 1111.
- Release JMP_EN, clock once. Verify counter resumes: 0000.

 


Figure 7: Reset overrides jump — RST = 1 and JMP_EN = 1 with ADDR = 1111, yet PC_OUT stays 0000.

7 Summary of Equations

For reference, the complete logic for each flip-flop bit i :

Signal	Equation
SET_i	$\overline{RST} \text{ AND } JMP_EN \text{ AND } ADDR[i]$
CLR_i	$RST \text{ OR } (JMP_EN \text{ AND } \overline{ADDR[i]})$
T_0	$\overline{JMP_EN}$
T_1	$\overline{JMP_EN} \text{ AND } Q_0$
T_2	$T_1 \text{ AND } Q_1$ (carry chain)
T_3	$T_2 \text{ AND } Q_2$ (carry chain)

8 What to Save

Your file must include the following subcircuit:

- ProgramCounter_TFF

9 Optional Extension

If you finish early:

1. **ROM integration.** Connect PC_OUT to your instruction ROM from Tutorial 13 and verify the PC steps through stored instructions automatically.
2. **Conditional branch.** Add external combinational logic that checks a register value and drives JMP_EN only when the condition is met (e.g. jump-if-zero/jump-if-not-zero [JZ/JNZ]).
3. **HALT.** Add a HALT input that freezes the PC (forces all T-inputs to 0 and disables set/clear).